

III B. Tech I Semester Regular Examinations, October/November - 2018**LINEAR IC APPLICATIONS****(Common to Electronics and Communication Engineering, Electronics and Instrumentation Engineering)**

Time: 3 hours

Max. Marks: 70

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)
 2. Answer **ALL** the question in **Part-A**
 3. Answer any **FOUR** Questions from **Part-B**
- ~~~~~

PART -A

1. a) What does the term “balanced output” mean? [2M]
- b) Define CMRR. [2M]
- c) What is an instrumentation amplifier? [3M]
- d) What is all-pass filter? [2M]
- e) Draw the pin diagram of 555 Timer. [3M]
- f) Define resolution of a convertor. [2M]

PART -B

2. a) Derive the expression for voltage gain of a single input, balanced output differential amplifier. [7M]
- b) Draw the circuit diagram of two-stage differential amplifier and explain it. [7M]
3. a) Explain about integrated circuit package types. [7M]
- b) Explain the following: [7M]
 - i) Input offset voltage
 - ii) Input offset current.
4. a) Draw the circuit diagram of log amplifier and explain its operation. [7M]
- b) Design an op-amp differentiator that will differentiate an input signal with $f_{\max} = 100$ Hz. [7M]
5. a) Design and plot the frequency response of a first order high pass filter for pass band gain of 2 and lower cut-off frequency of 2 KHz. . [7M]
- b) Explain the operation of Four-Quadrant Multiplier. [7M]
6. a) Draw the functional diagram of astable multivibrator using 555 timer and explain its operation. [7M]
- b) Derive the expression for lock in range. [7M]
7. a) Explain about IC 1408 D/A convertor. [7M]
- b) Explain about counter type A/D convertor. [7M]



III B. Tech I Semester Regular Examinations, October/November - 2018**LINEAR IC APPLICATIONS****(Common to Electronics and Communication Engineering, Electronics and Instrumentation Engineering)**

Time: 3 hours

Max. Marks: 70

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)
 2. Answer **ALL** the question in **Part-A**
 3. Answer any **FOUR** Questions from **Part-B**
- ~~~~~

PART -A

1. a) Define differential amplifier? [2M]
- b) List out the temperature ranges for ICs. [2M]
- c) What is meant by buffer? [2M]
- d) Define band pass and band reject filter. [3M]
- e) List the basic building blocks of PLL. [3M]
- f) Write the significance of linearity in a convertor. [2M]

PART -B

2. a) Derive the expression for voltage gain of a dual input, unbalanced output differential amplifier. [7M]
- b) Draw the circuit diagram of level translator using emitter follower and explain it. [7M]
3. a) Draw the high frequency model of an op-amp with single break frequency and analyze the open loop voltage gain as a function of frequency. [7M]
- b) Explain the following: [7M]
 - i) Slew rate
 - ii) thermal drift.
4. a) Draw the circuit diagram of sample and hold circuit. Explain its operation. [7M]
- b) Find R_I and R_F in the lossy integrator so that peak gain is 20 dB and the gain is 3 dB down from its peak value when $\omega = 10000$ rad/s. use a capacitance of 0.01 μ F. [7M]
5. a) Draw the circuit diagram of second order generalized active filter and derive the expression for transfer function. [7M]
- b) Design a second order Butterworth low-pass filter having a upper cut-off frequency of 1 kHz. [7M]
6. a) Draw the functional diagram of monostable multivibrator using 555 timer and explain its operation. [7M]
- b) Explain the following: [7M]
 - i) PLL used as Frequency translation
 - ii) PLL used as AM demodulator
7. a) Explain about weighted resistor DAC and write the drawbacks of it. [7M]
- b) Explain about successive approximation ADC. [7M]



III B. Tech I Semester Regular Examinations, October/November - 2018**LINEAR IC APPLICATIONS****(Common to Electronics and Communication Engineering, Electronics and Instrumentation Engineering)**

Time: 3 hours

Max. Marks: 70

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)
 2. Answer **ALL** the question in **Part-A**
 3. Answer any **FOUR** Questions from **Part-B**
- ~~~~~

PART -A

1. a) What is level translator circuit? [2M]
- b) Define PSRR. [2M]
- c) List out the applications of comparator. [2M]
- d) Define notch filter. [2M]
- e) List out the applications of VCO. [3M]
- f) Find the resolution and dynamic range of a D/A convertor, if the maximum peak to peak output voltage is 5 V and the input signal is a 10 bit word. [3M]

PART -B

2. Draw the circuit diagrams of all four differential amplifier configurations and write the expressions for voltage gain, input resistance and output resistance. [14M]
3. a) Draw the block diagram of a typical op-amp and explain it. [7M]
- b) What is meant by an integrated circuit? Give the classification of ICs based on number of components integrated on the same chip. [7M]
4. a) Explain the operation of square wave generator using op-amp. [7M]
- b) Design an adder circuit using an op-amp to get the output expression as $V_0 = -(0.1 V_1 + V_2 + 10 V_3)$. [7M]
5. a) Draw the circuit diagram of first order high-pass filter using op-amp and explain its operation. [7M]
- b) Design a wide-band pass filter having $f_l = 400$ Hz, $f_h = 2$ kHz and a pass band gain of 4. Find the value of Q of the filter. [7M]
6. a) Explain the operation of FSK generator using 555 Timer. [7M]
- b) Draw the block diagram of 565 PLL and explain it. [7M]
7. a) Explain about R-2R DAC. [7M]
- b) Explain about Dual-Slope ADC. [7M]



III B. Tech I Semester Regular Examinations, October/November - 2018**LINEAR IC APPLICATIONS****(Common to Electronics and Communication Engineering, Electronics and Instrumentation Engineering)**

Time: 3 hours

Max. Marks: 70

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)
 2. Answer **ALL** the question in **Part-A**
 3. Answer any **FOUR** Questions from **Part-B**
- ~~~~~

PART -A

1. a) List out the four differential amplifier configurations. [2M]
- b) Write the difference between digital ICs and linear ICs. [3M]
- c) Draw the ideal and practical transfer characteristics of a comparator. [3M]
- d) Draw the Sample and Hold Circuit. [2M]
- e) Define capture range and lock in range. [2M]
- f) What is the difference between A/D and D/A convertor? Give one application of each one. [2M]

PART -B

2. a) Draw the circuit diagram of differential amplifier in common mode configuration and explain it. [7M]
- b) Derive the expression for input resistance and output resistance of a dual input, unbalanced output differential amplifier. [7M]
3. a) What is an operational amplifier? List out the ideal characteristics of operational amplifier. [7M]
- b) What is meant by frequency compensation? Explain about pole-zero compensation. [7M]
4. a) Explain the operation of triangular wave generator using op-amp. [7M]
- b) Explain about V to I convertor using op-amp. Write the applications of it. [7M]
5. a) Draw the circuit diagram of first order low-pass filter using op-amp and explain the operation. [7M]
- b) Design a second order Butterworth high-pass filter having a lower cut-off frequency of 1 kHz. [7M]
6. a) Draw the circuit diagram of Schmitt trigger using 555 timer and explain its operation. [7M]
- b) Give the block diagram of IC 566 VCO and explain its operation. [7M]
7. a) Explain about Inverted R-2R ladder DAC. [7M]
- b) Explain the important specifications of D/A and A/D convertors. [7M]

